

Group A and Group B

1. Professor Calculus wants to construct a single port memory *VEDA* of dimension 32×32 . This means that the depth of the memory is 32 and the width of the memory is 32 bits. A block diagram of this memory is shown in Figure 1. This memory operates into two different modes: *scribble* when *mode*=0 and *interpret* when *mode*=1. In *scribble* mode, the input data is written to the memory and driven on the data output. In *interpret* mode, the data previously written in the memory will be provided the output. In both the cases, the data will appear at the output port after one clock cycle delay of providing address value. Help professor Calculus to construct this memory by writing its Verilog code.

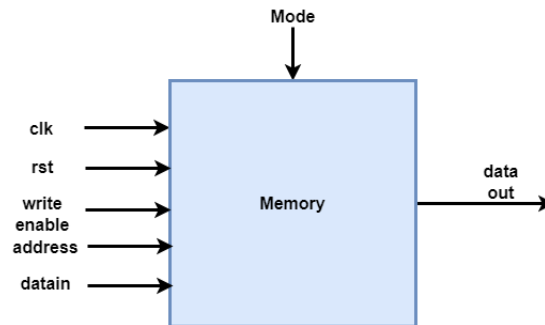


Figure 1: Veda Memory

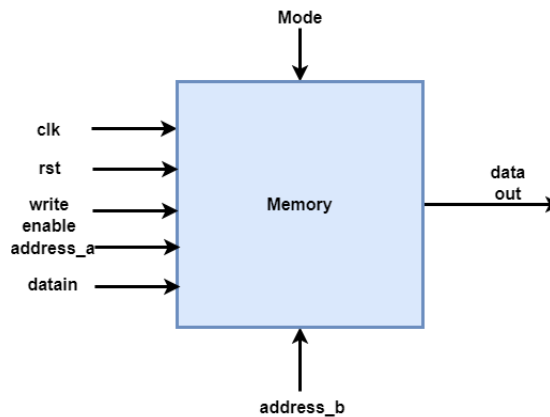


Figure 2: Veda Memory with two address ports

2. The next objective is to create a modified version of *VEDA* as shown in Figure 2. Here the memory has two different address ports *address_a* and *address_b*. The *address_a* port is used to write in to the memory and *address_b* is used to read from the memory. Write a Verilog code for this architecture. Note that *address_a* and *address_b* can not be of the same value.